Play-doh Circuits for kids (https://www.youtube.com/watch?v=VcdqBmFETNw)

Make one eye light up? How to make two eye light up with one battery?

Select one that you like to light up?

Did All the LEDs Light up?

Select the light that is appropriate for the ducks to cross?

Select the light that is appropriate for the cars to stop?

Select the light that is a warning to stop?

Did all the LEDs light up? Can you tell which one is not working?
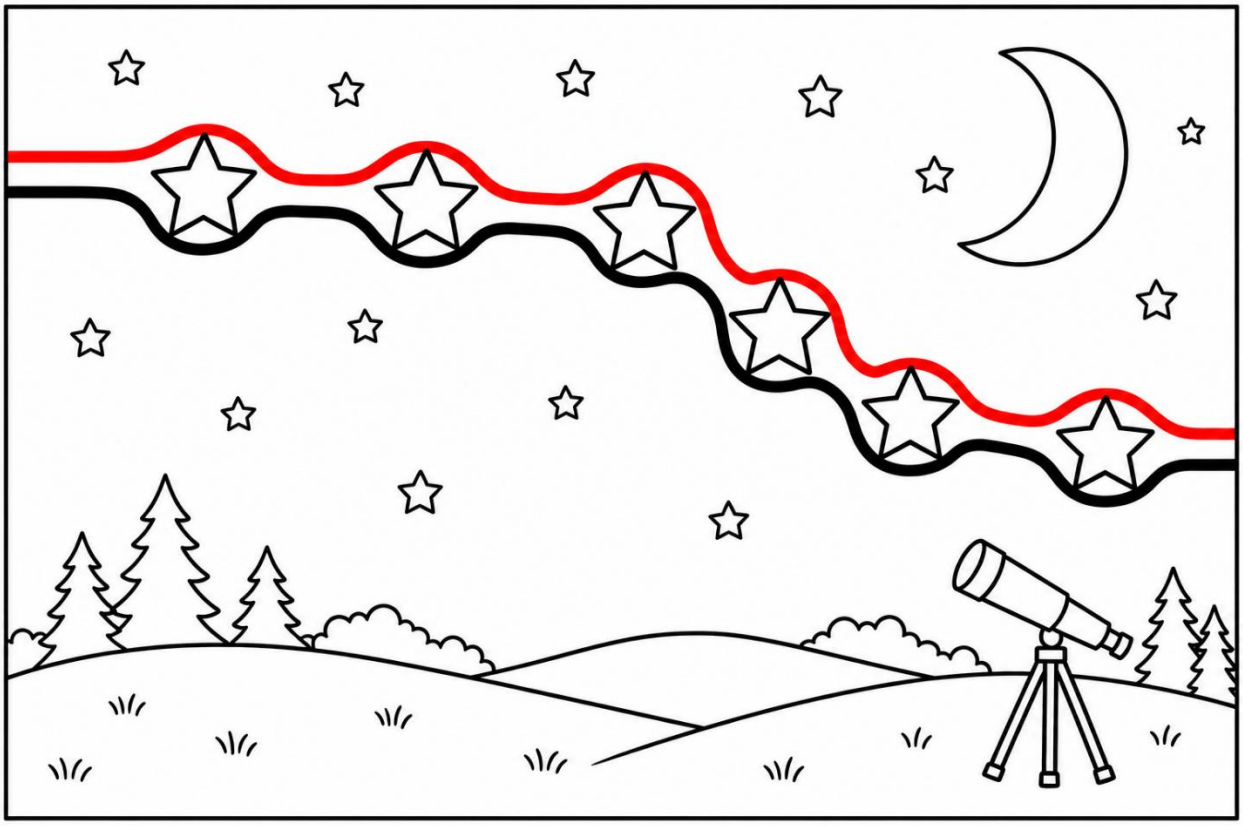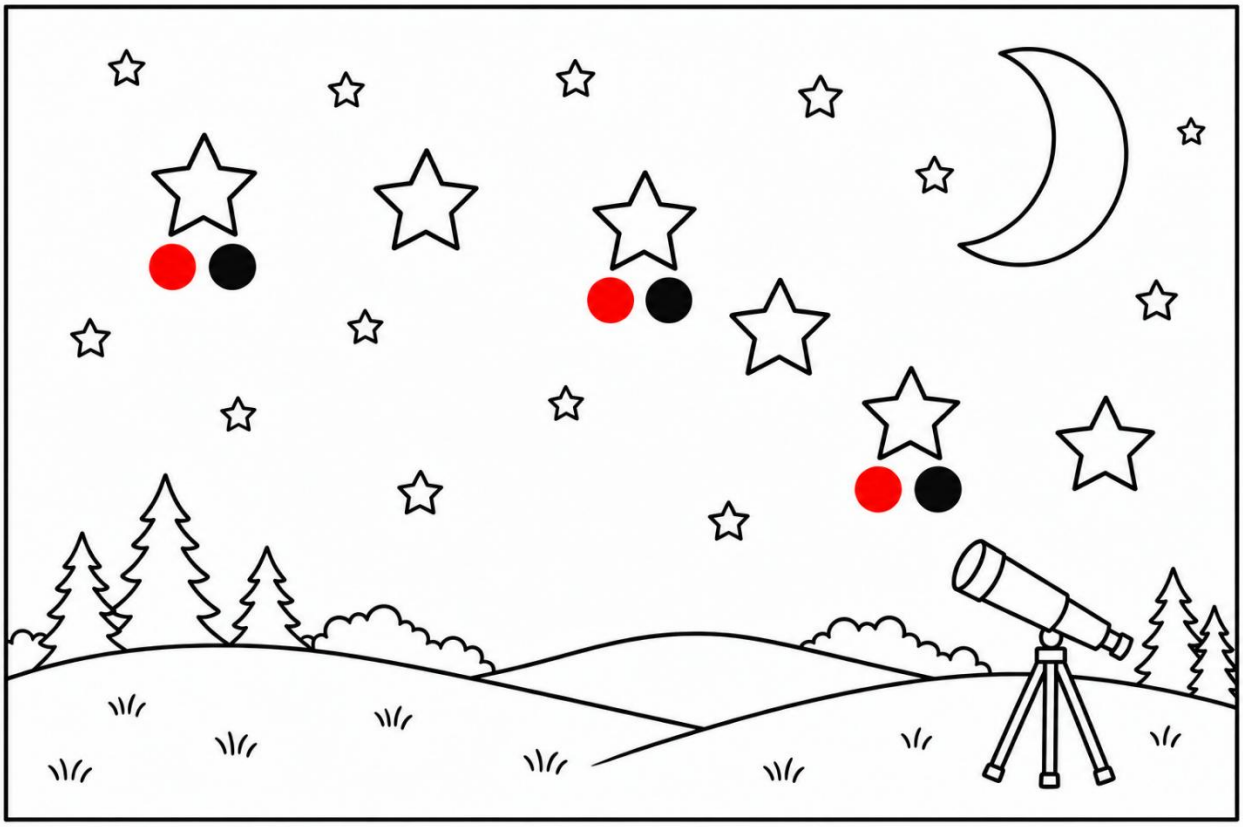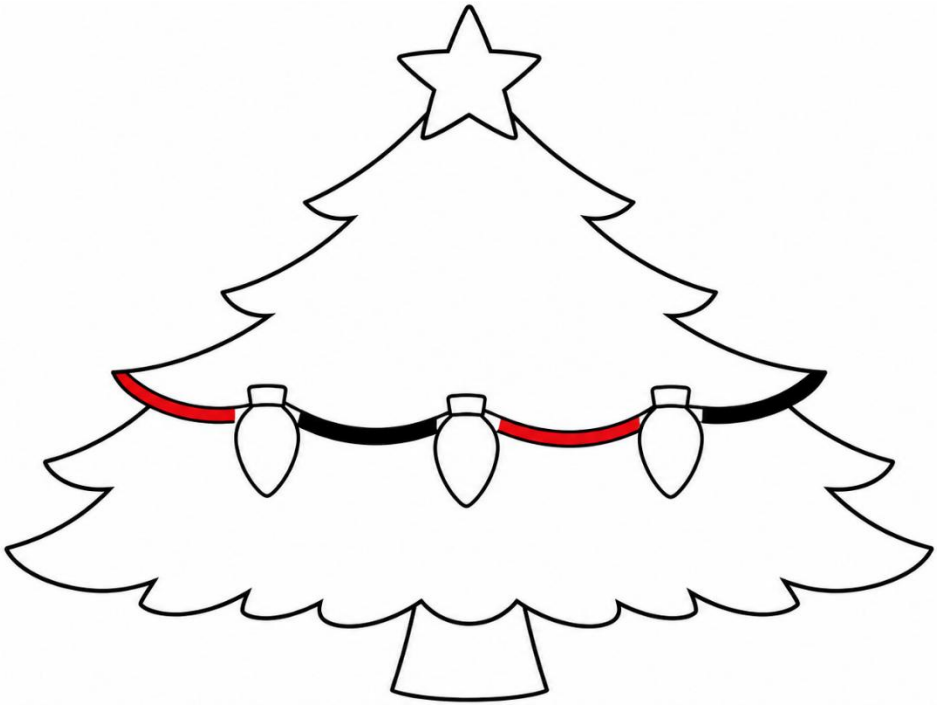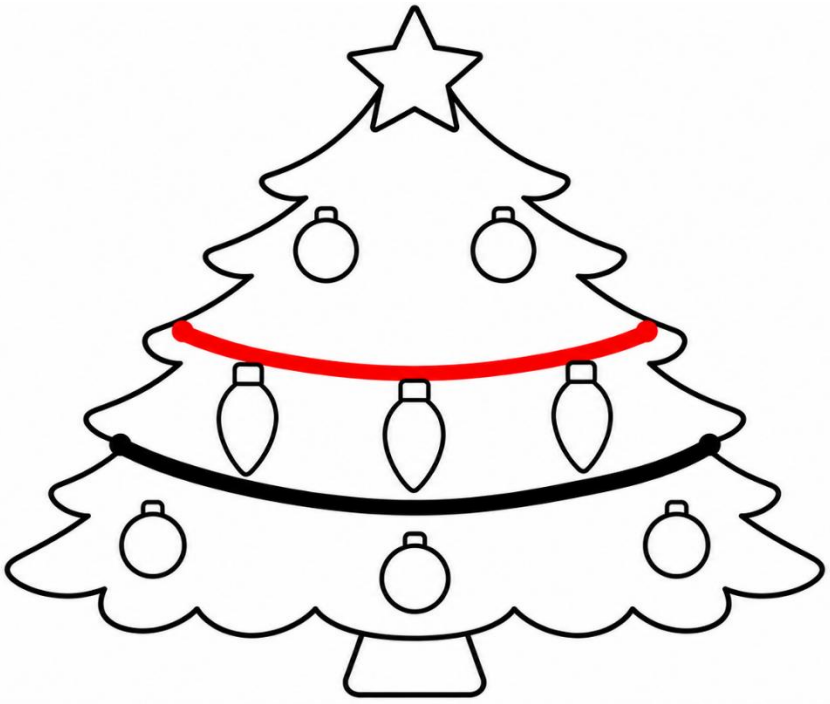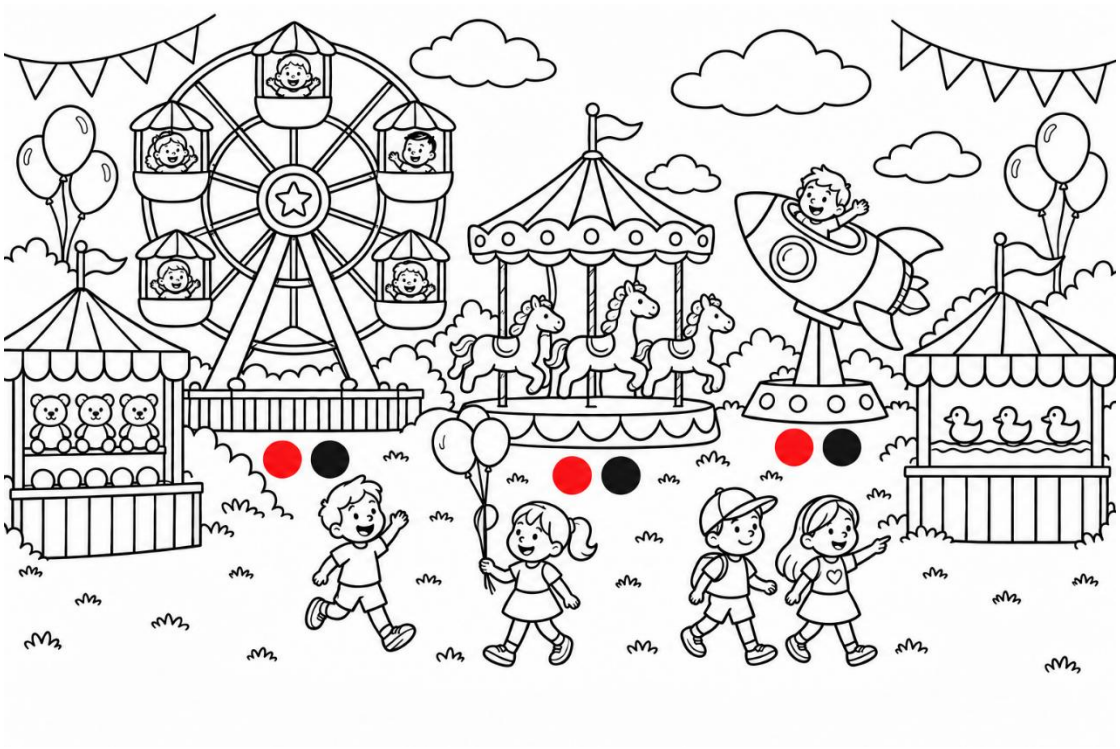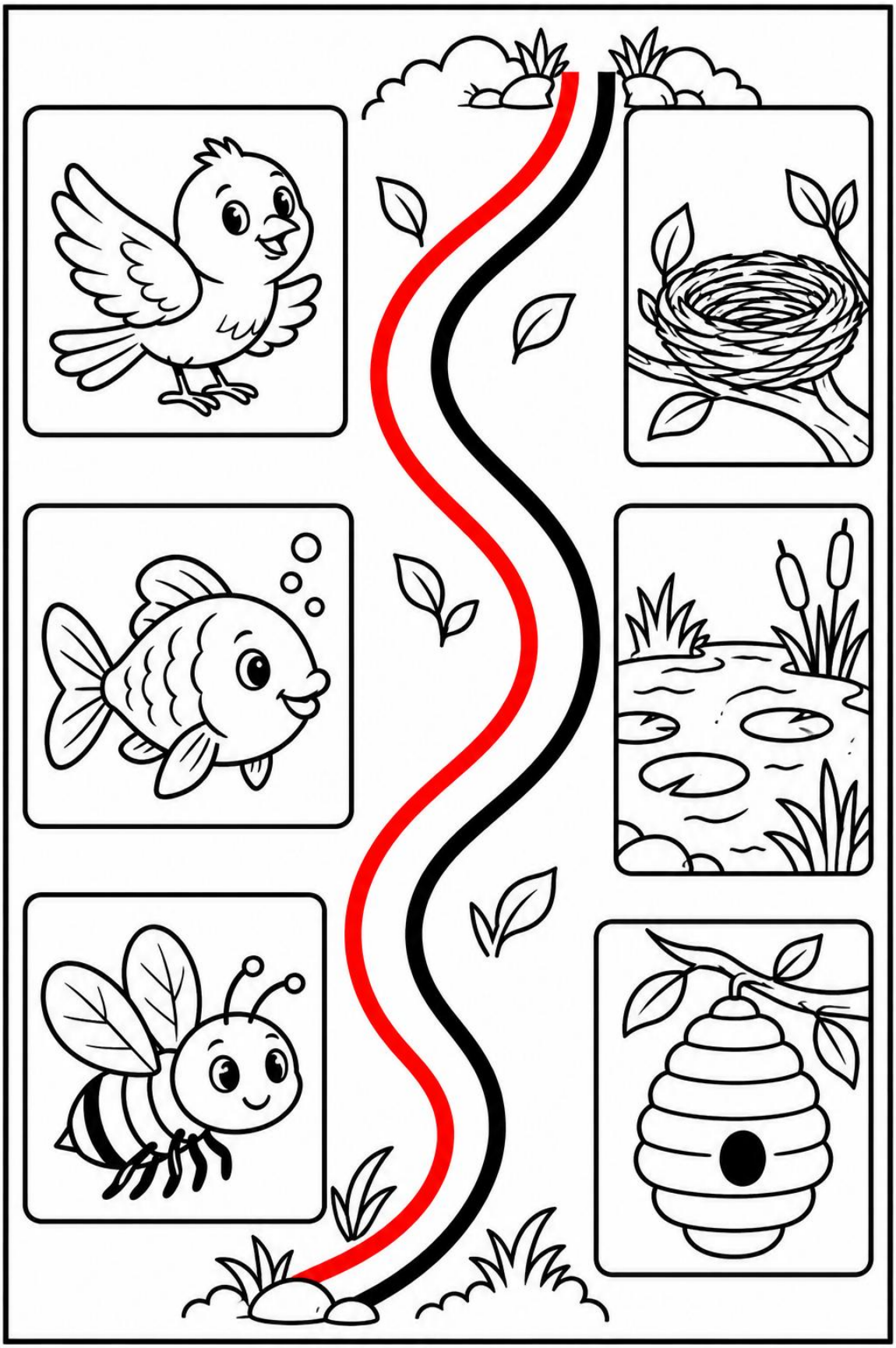
Did all the LEDs light up Can you tell which one is not working?